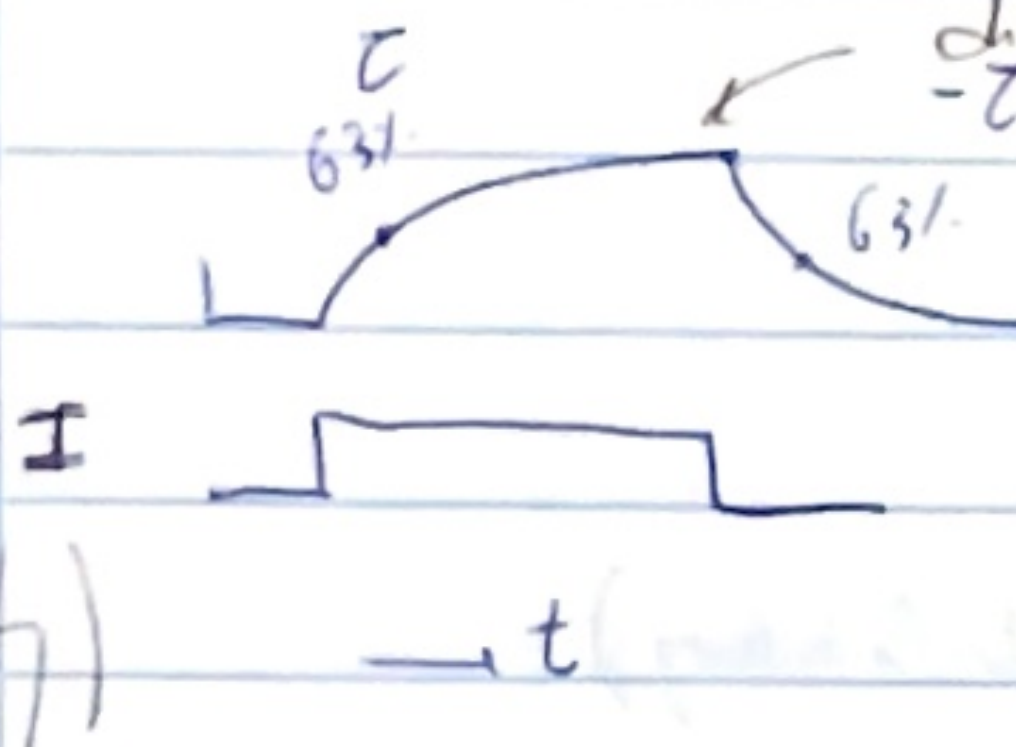


WEEK 3

because it behaves as a RC circuit

this cell can be regenerated =

BACKGROUND ON ELECTRICITY



V (Voltage) RC system
 $I \rightarrow RC, V = 0.63 IR$
 $t \rightarrow 0, V = 0$
 $t \rightarrow \infty, V = IR$



gate of membrane

$V(t) = IR(1 - e^{-t/RC})$ $RC = \tau$ constant

where its

$\tau \gg \rightarrow$ long time to charge/discharge
 $\tau \ll \rightarrow$ less time to charge/discharge

$I = RC$ Kirchhoff law

TEMPORAL SUMMATION

it is due to the fact that we have τ constant



electrical memory


IR is the maximum you can get

magnetic inputs

not too long so it sums up (in the order of τ)



Resting potential $-70mV$

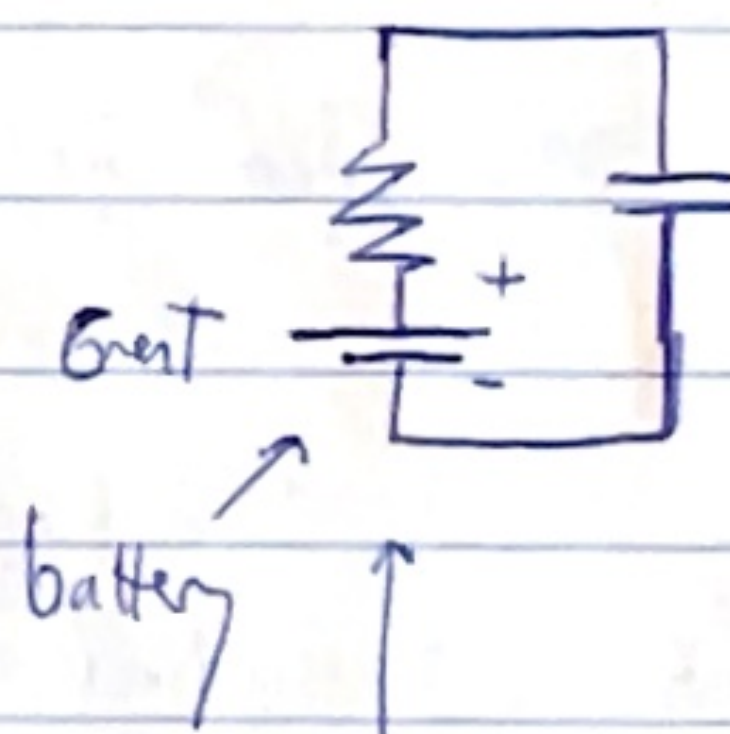

I add a battery is the resting potential

hyperpolarization
 depolarization

KIRCHOFF

$C \frac{dV}{dt} + \frac{V}{R} = I \rightarrow$ injected current


capacitance current

resistor current



regenerated by

(the gate of cell)

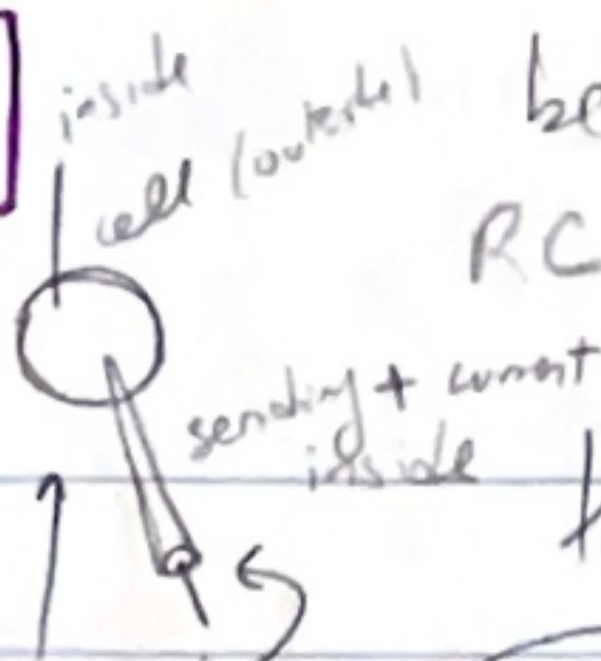

because it behaves as a RC circuit

this cell can be regenerated =

the cell is not a resistor

(Intensity)

otherwise the voltage would be linear

τ_m

membrane time

Constant $t = RC = \tau_m$

controls how the V $\uparrow$ or $\downarrow$


τ short, V takes short

electrical elements

τ long $\rightarrow$ takes long

tells you about the memory of the cell


THE SYNAPTIC POTENTIAL

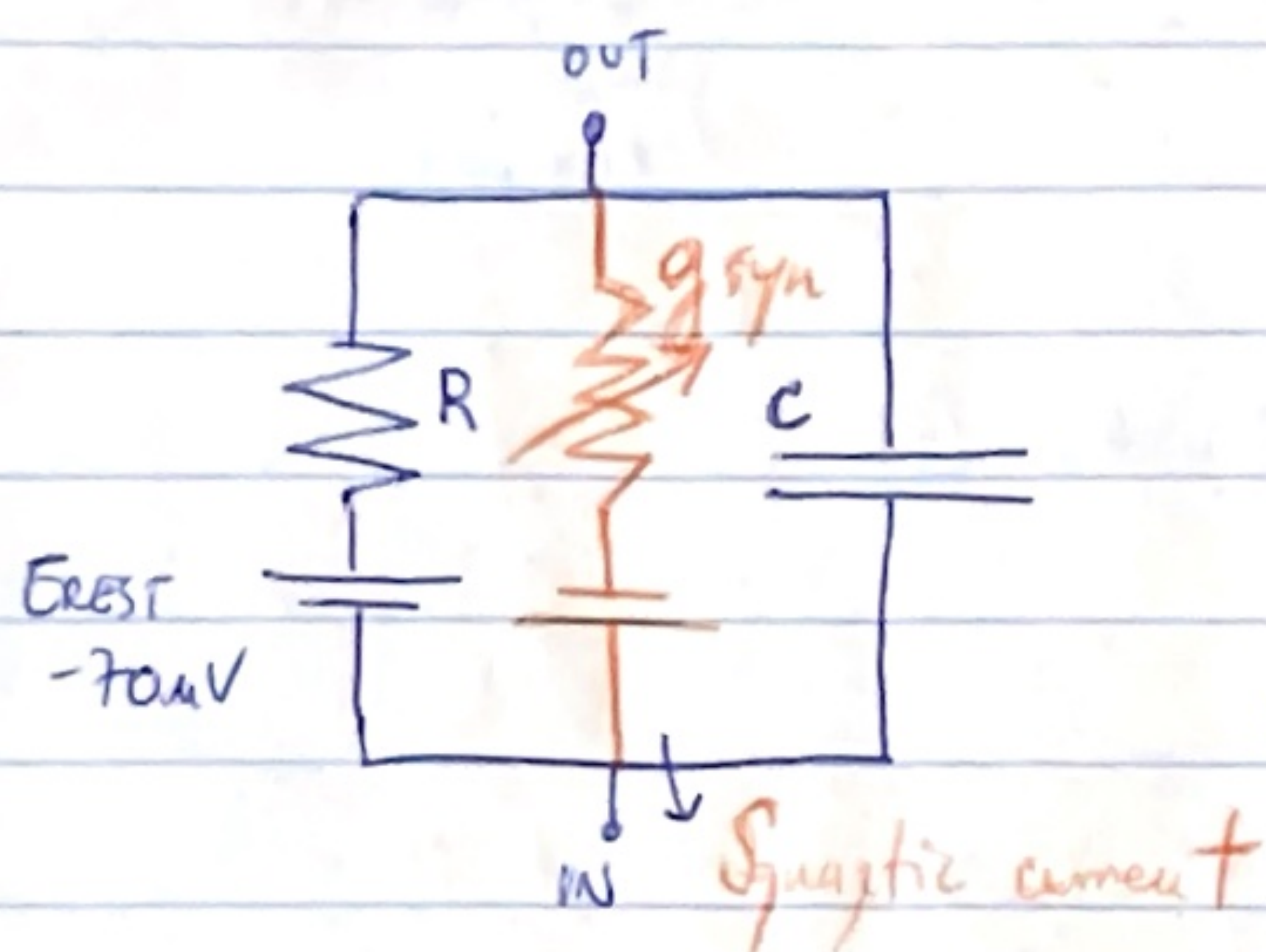

Neuron as variable RC circuits

Synapse on the electrode
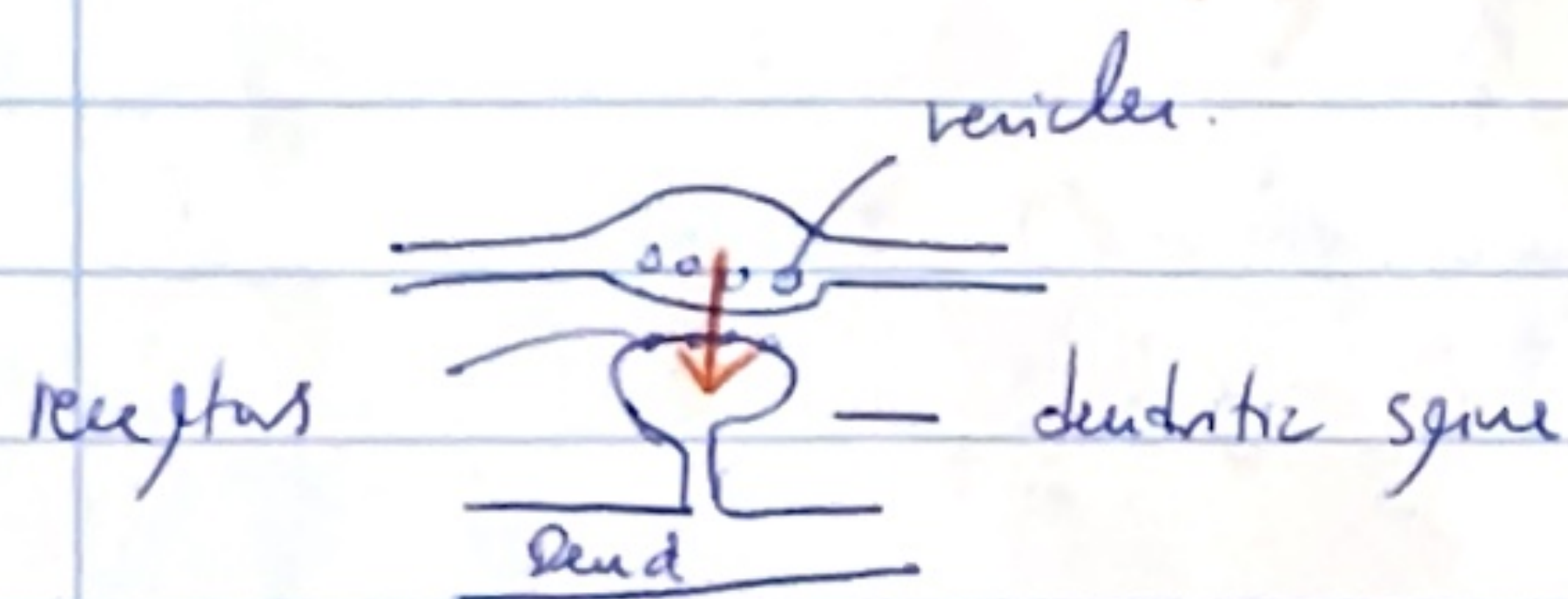
$$R \cdot C = \tau_m \approx 20 \mu\text{sec}$$




Synapse $\rightarrow$ open ion channels
depending which one
the direction of the
flow






each channel has a conductance $\rightarrow$ Total conductance $= \frac{1}{R}$
(same) $g_r + g_r$
don't depend on anything

conductance

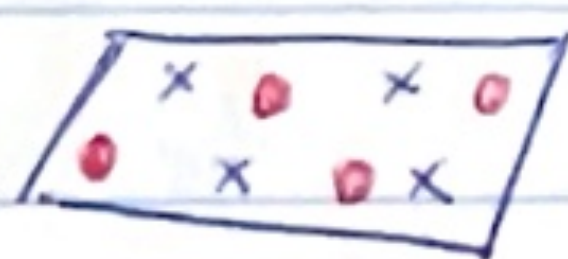

Synaptic channels $\rightarrow$ Ion channels $\rightarrow$ g_{synapse}
open if transmitters are being released


THE SYNAPTIC BATTERY

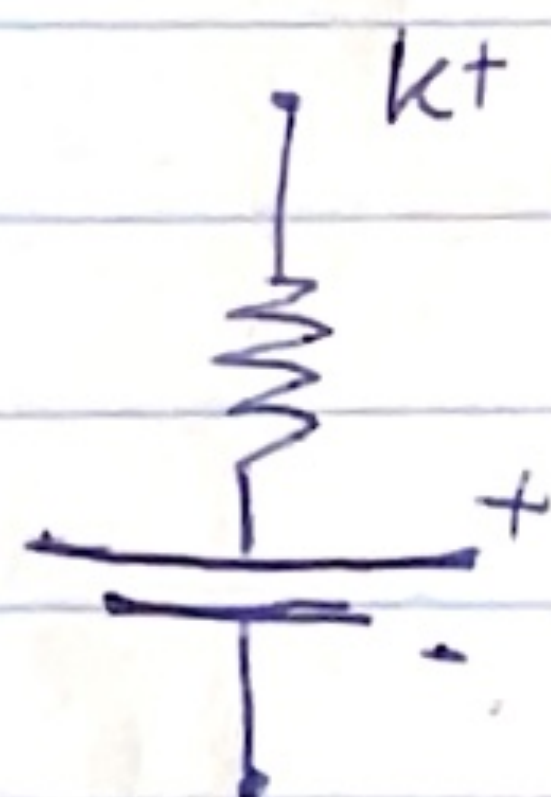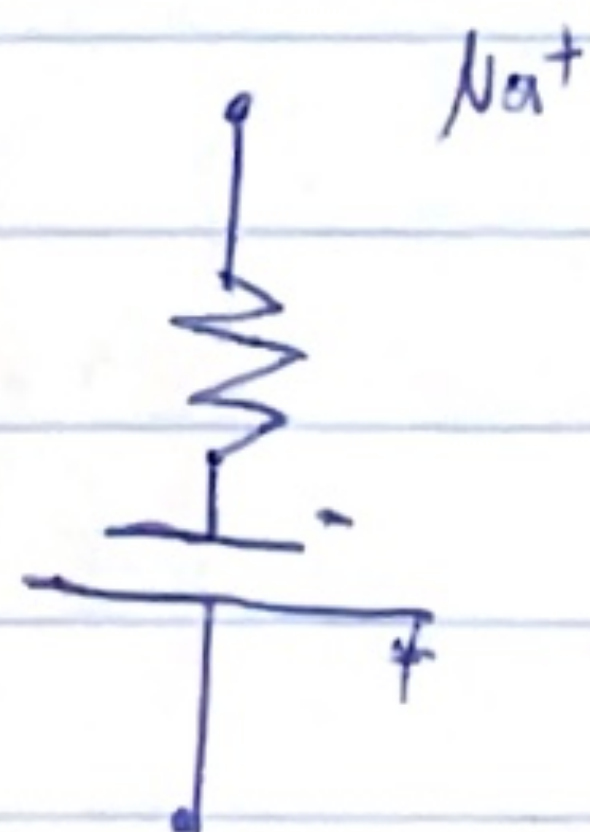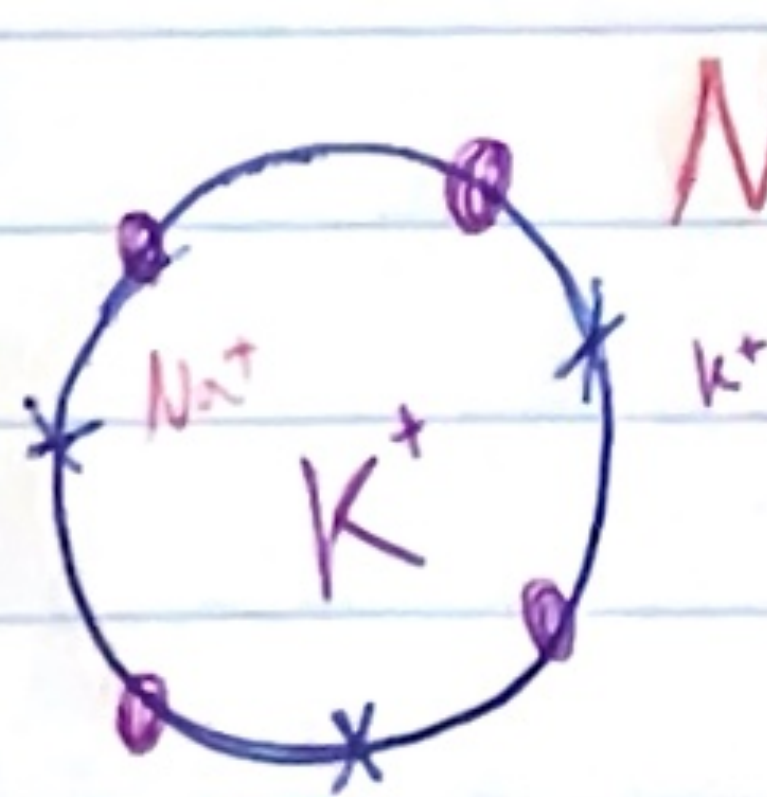

PSP

synaptic current

$g = \text{conductance}$

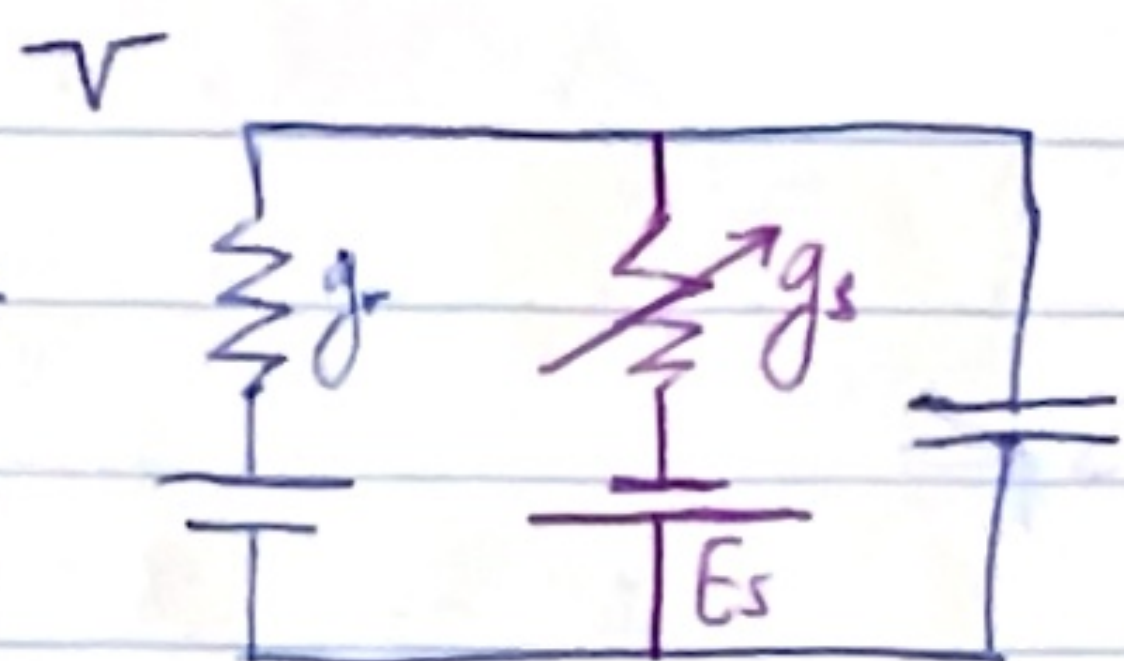

$$0 = \underbrace{C \frac{dV}{dt}}_{\text{capacitance current}} + \underbrace{g_r (V - E_r)}_{\text{leakage current}} + g_s (V - E_s)$$

Ohm

Kirchoff's law

Conductance

Kirchoff's law (?)


$$V(t) = \frac{g_r E_r + g_s E_s}{g_r + g_s}$$

→ In the nervous system the voltage changes related to batteries.
(No current from outside)




positive battery
↓

Na^+ (+ ions get in)

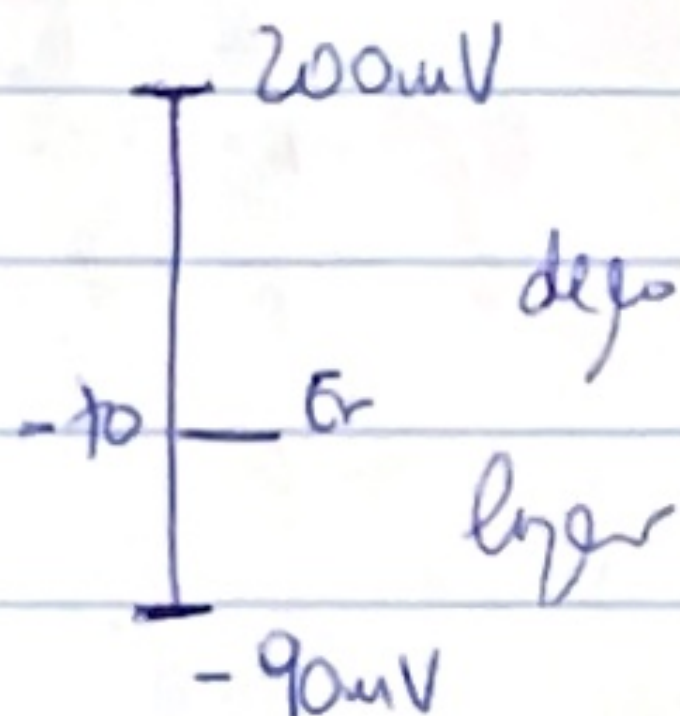

max or minimum voltages are the batteries.

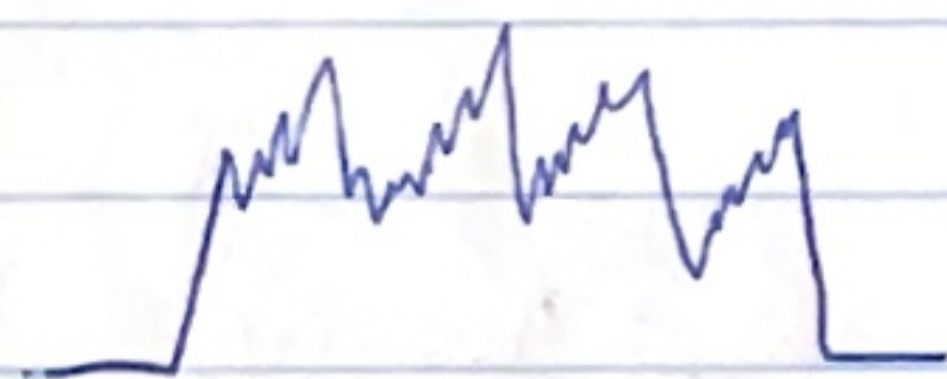Inhibitory postsynaptic potential IPSP
excitatory " " " EPSP



temporal summation (IPSP + EPSP)